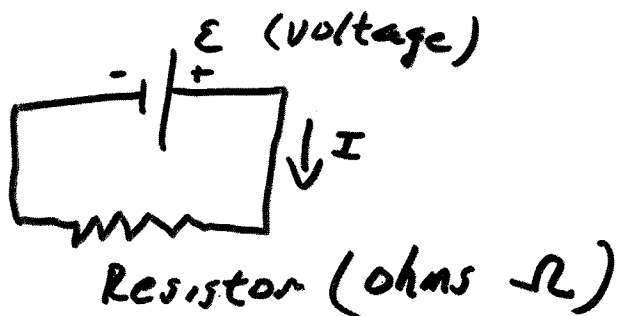


## Read 13.4

### 02L group problems updated Group tomorrow - circuits Review


Current  $I = \frac{\mathcal{E}}{R}$  (Amps)



OHM's Law  $\Delta V = IR$

loop rule: around any closed loop  
sum of voltage rises = sum  
of voltage drops

Resistors in series

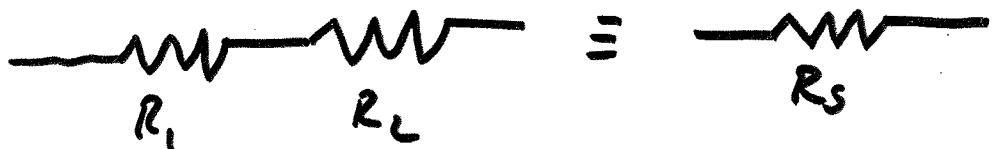


$$R_s = R_1 + R_2$$

same current flowing through them

Problem: A  $3\Omega$ , a  $6\Omega$ , and a  $9\Omega$  resistor are placed in series and connected to a  $12\text{ V}$  battery?

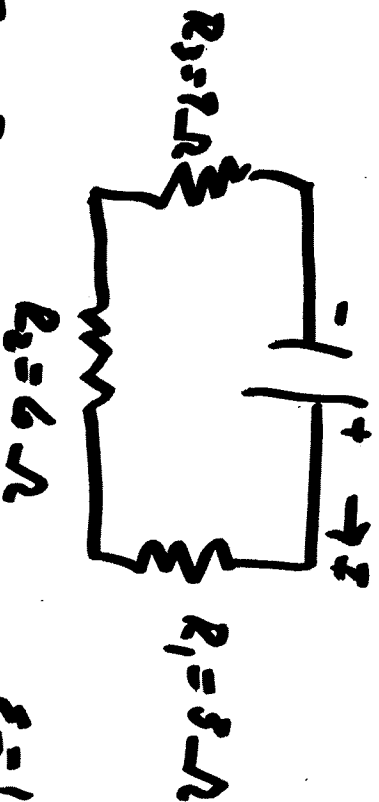
(a) What is the current flowing through each resistor?



$$R_s = R_1 + R_2 + R_3$$

$$= 3\Omega + 6\Omega + 9\Omega = 18\Omega$$

$$\mathcal{E} = 12\text{ V}$$

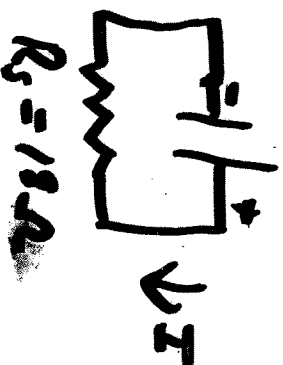


$$\mathcal{E} = IR$$

$$I = \frac{\mathcal{E}}{R} = \frac{12\text{ V}}{18\Omega} = \underline{0.67\text{ A}}$$

all have same  
current

Problem: A  $3\Omega$ , a  $6\Omega$ , and a  $9\Omega$  resistor are placed in series and connected to a 12 V battery?

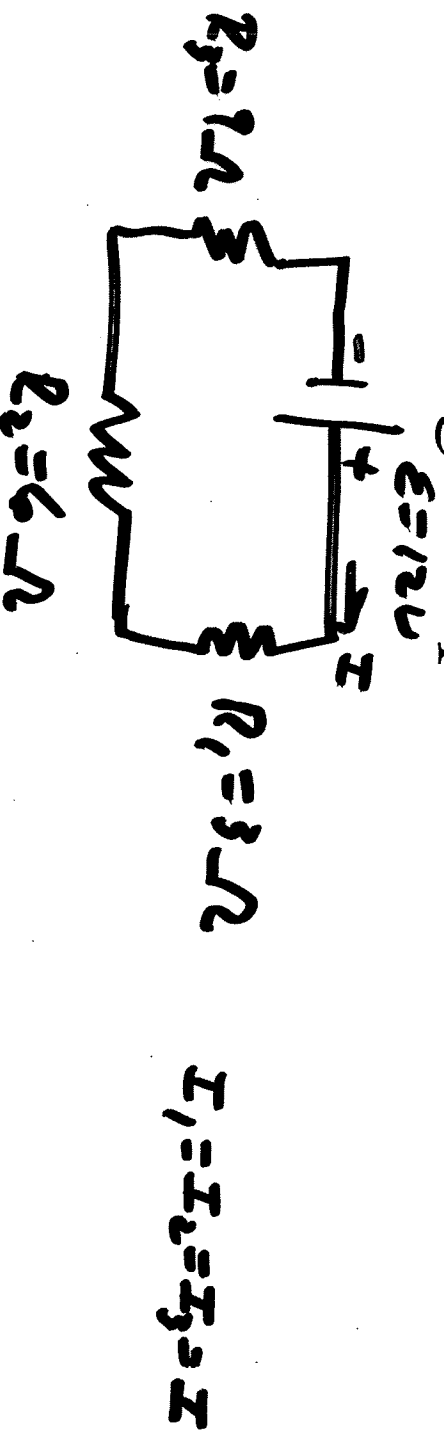(b) What is the voltage drop across each resistor?



$$\Delta V_1 = I_1 R_1 = (1.67A)(3\Omega) = 2V$$

$$\Delta V_2 = I_2 R_2 = (1.67A)(6\Omega) = 4V$$


$$\Delta V_3 = I_3 R_3 = (1.67A)(9\Omega) = 6V$$

$$\Delta V_1 + \Delta V_2 + \Delta V_3 = \underline{12V}$$
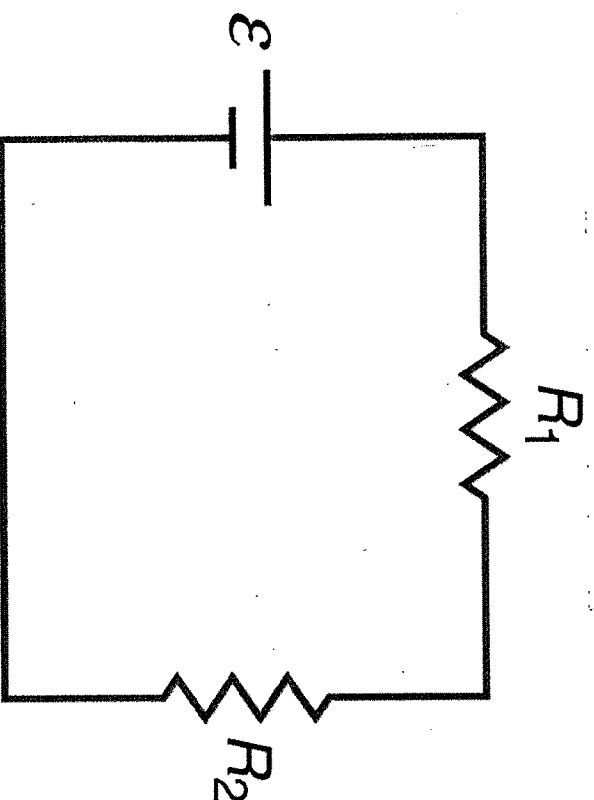
## Interactive Question




Two resistors are connected in series with a battery as shown.  $R_1$  is less than  $R_2$ . Which of the two resistors has the greater current flowing through it?



- A)  $R_1$
- B)  $R_2$
- C) They have the same current
- D) More information is needed
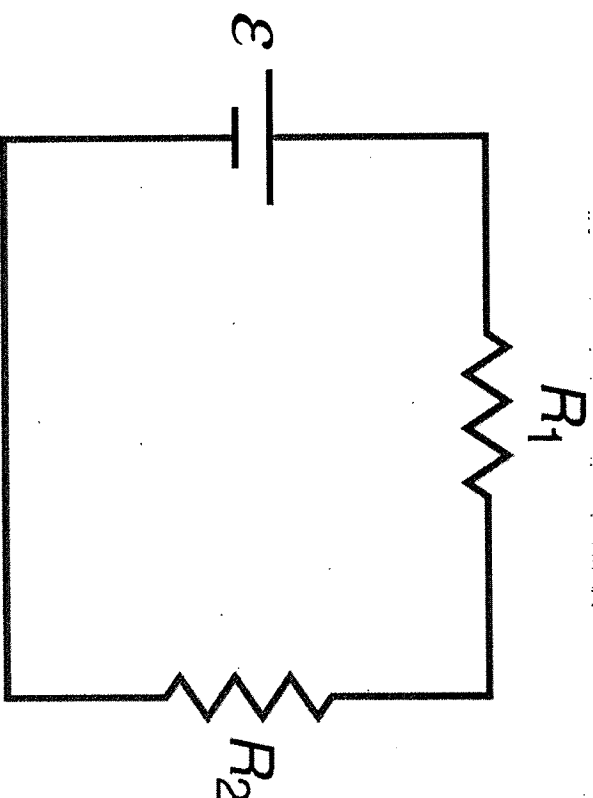
## Interactive Question

Two resistors are connected in series with a battery as shown.  $R_1$  is less than  $R_2$ . Which of the two resistors has the greatest voltage difference across it?



- A)  $R_1$
- B)  $R_2$
- C) They have the same voltage difference
- D) More information is needed


Problem: An ideal battery has a voltage of 9.0 volts and is attached to a  $20\ \Omega$  external resistor. The battery has an internal resistance of  $1\ \Omega$ .

- A) What current is flowing through the circuit?  
 B) What is the terminal voltage of the battery?

$$1) R_s = R_1 + R_2 = 1\ \Omega + 20\ \Omega = \underline{21\ \Omega}$$

$$\mathcal{E} = IR$$
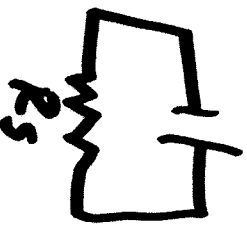
$$I = \frac{\mathcal{E}}{R} = \frac{9V}{21\ \Omega}$$




$$= .429\ A$$

$$B) V_T = \mathcal{E} - IR_1$$

$$9V - (.429\ A \times 1\ \Omega)$$


$$8.571\ V \approx \underline{8.6\ V}$$

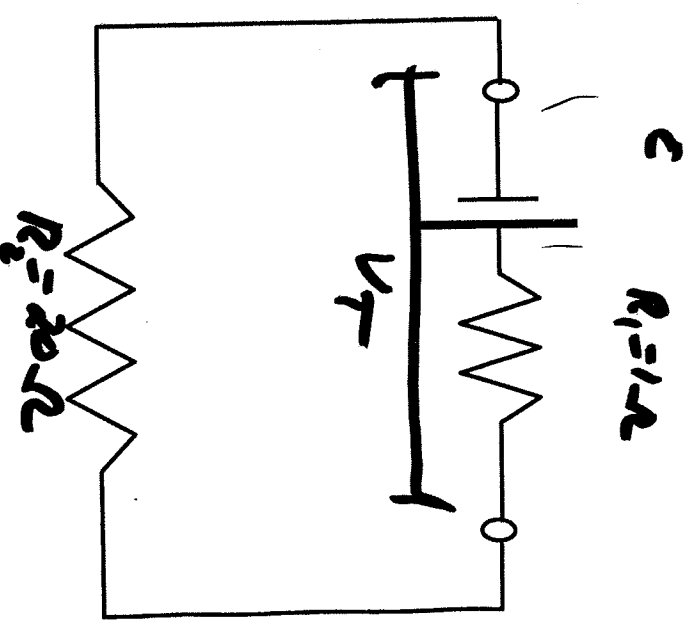


(B)
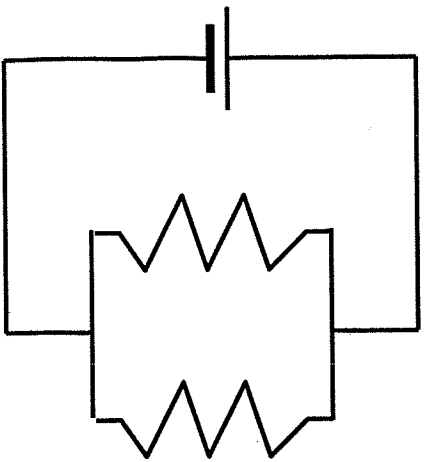
## Interactive Question


Which of the following circuits are identical?



(A)

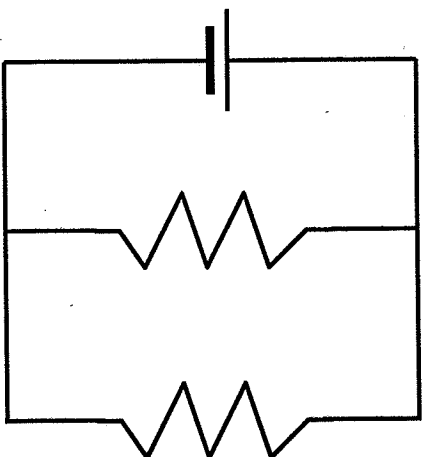

(B)

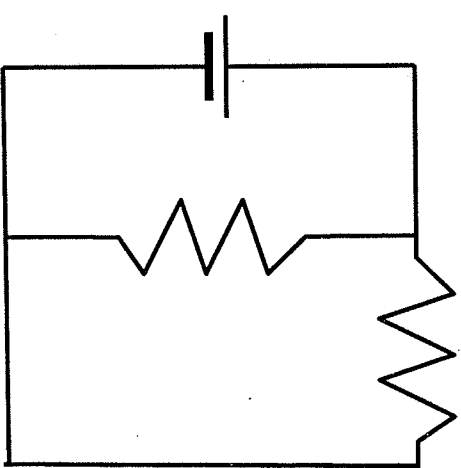


(C)

- A) (A) and (B) only
- B) (B) and (C) only
- C) (A) and (C) only
- D) (A), (B), and (C)
- E) None of the above

Problem: A  $3\ \Omega$ , a  $6\ \Omega$ , and a  $9\ \Omega$  resistor are placed in parallel and connected to a  $12\ \text{V}$  battery?

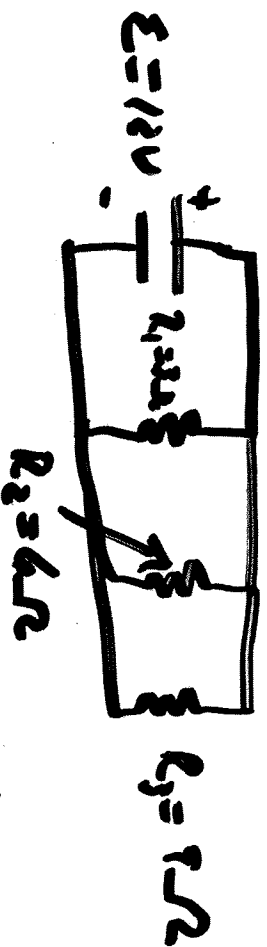(a) What is the total current flowing through the system?



$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{3\ \Omega} + \frac{1}{6\ \Omega} + \frac{1}{9\ \Omega} = \frac{4}{18\ \Omega} + \frac{3}{18\ \Omega} + \frac{2}{18\ \Omega}$$

$$\frac{1}{R_p} = \frac{11}{18\ \Omega} \quad R_p = \frac{18\ \Omega}{11} = 1.6\ \Omega$$

$$I = \frac{\mathcal{E}}{R_p} \quad \mathcal{E} = \frac{12\text{V}}{1.6\ \Omega} = 7.5\ \text{A}$$

$$= \underline{\underline{7.5\ \text{A}}}$$



Problem: A  $3\ \Omega$ , a  $6\ \Omega$ , and a  $9\ \Omega$  resistor are placed in parallel and connected to a  $12\text{ V}$  battery?

(b) What is the current in each resistor? ?

$$I_1 = \frac{\Delta V_1}{R_1} = \frac{12\text{ V}}{3\ \Omega} = 4\text{ A}$$

$$I_2 = \frac{\Delta V_2}{R_2} = \frac{12\text{ V}}{6\ \Omega} = 2\text{ A}$$

note

$$\Delta V_1 = \Delta V_2 = \Delta V_3 = \mathcal{E}$$



$$I_3 = \frac{\Delta V_3}{R_3} = \frac{12\text{ V}}{9\ \Omega} = 1.33\text{ A}$$

$$I_1 + I_2 + I_3 = \underline{\underline{7.33\text{ A}}}$$

(D)
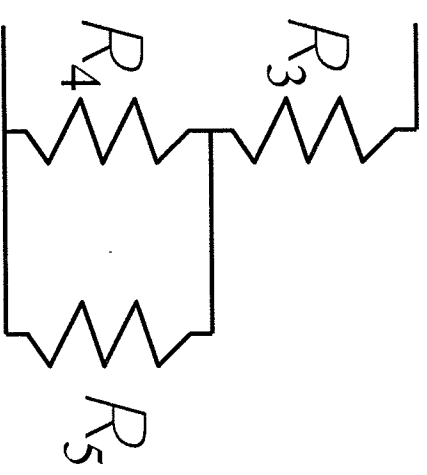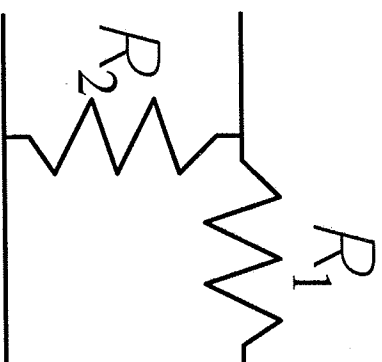
## Interactive Question

Consider the two circuits on the right. Which of the following statements is true?



- A)  $R_1$  and  $R_2$  are in parallel.  $R_3$  and  $R_4$  are in series.
- B)  $R_4$  and  $R_5$  are in parallel.  $R_3$  and  $R_4$  are in series.
- C)  $R_1$  and  $R_2$  are in series.  $R_3$  and  $R_4$  are in series.
- D)  $R_1$  and  $R_2$  are in parallel.  $R_4$  and  $R_5$  are in parallel.
- E)  $R_1$  and  $R_2$  are in series.  $R_4$  and  $R_5$  are in parallel.