

Read
Finish Chp 13
14.1-14.2


Review



series

$$R_s = R_1 + R_2$$

same I
Different V
 R_s larger

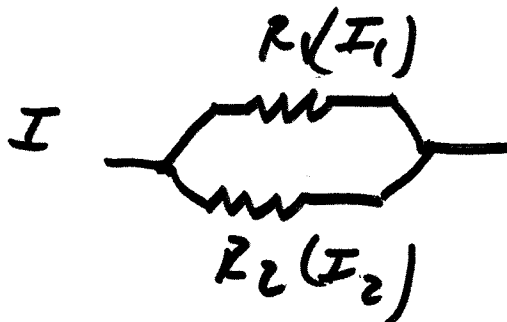

parallel
 $I = I_1 + I_2$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

same V
Different I
 R_p smaller

ex

$$R_1 = 2 \Omega$$
$$R_2 = 2 \Omega$$

$$R_s = 2 \Omega + 2 \Omega = 4 \Omega$$

$$\frac{1}{R_p} = \frac{1}{2 \Omega} + \frac{1}{2 \Omega} = \frac{1}{1 \Omega} \quad R_p = 1 \Omega$$


note parallel
same voltage so if R_1 large I small
 R_2 small I large

Interactive Question

C

In the circuit shown, R_3 is greater than R_2 , and R_2 is greater than R_1 . $\mathcal{E}$ is the electromotive force of the battery whose internal resistance is negligible. Which of the three resistors has the greatest current flowing through it?

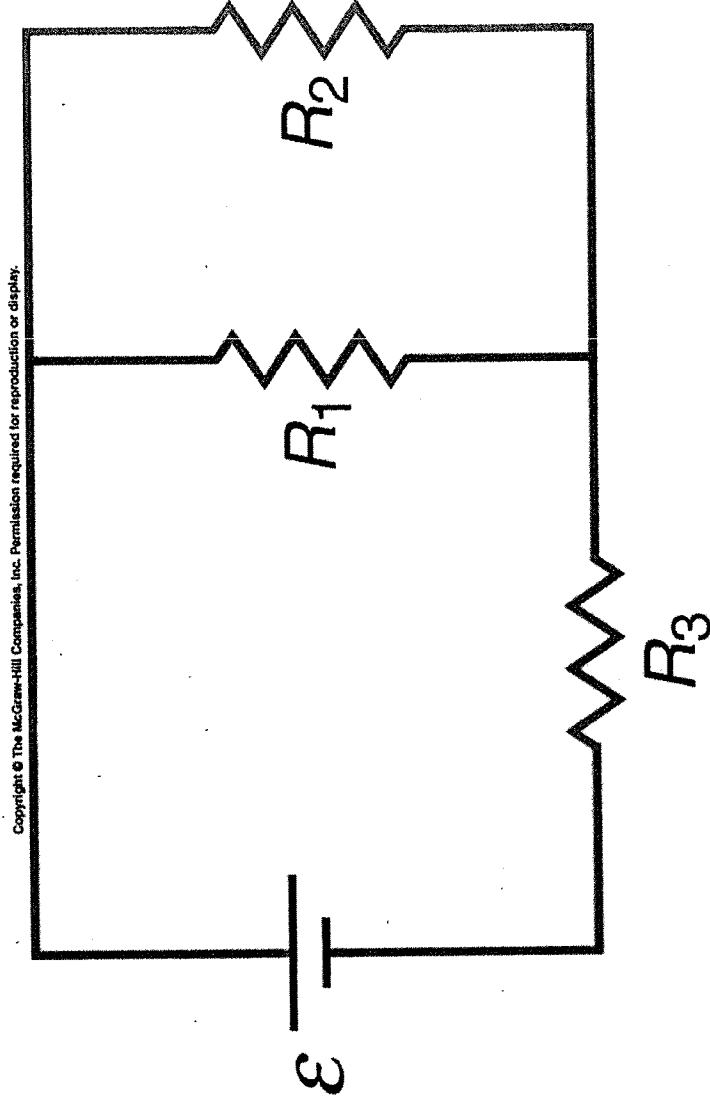
- A) R_1
- B) R_2
- C) R_3
- D) R_1 and R_2 are equal, and greater than R_3
- E) They are all equal



A

Interactive Question

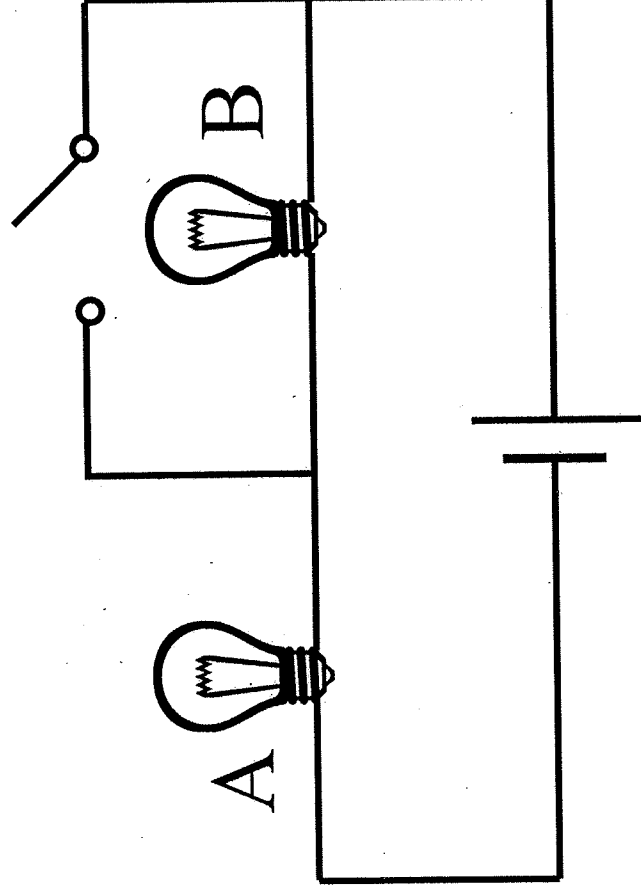
The circuit below consists of two identical light bulbs burning with equal brightness and a single 12 V battery. When the switch is closed, the brightness of bulb A



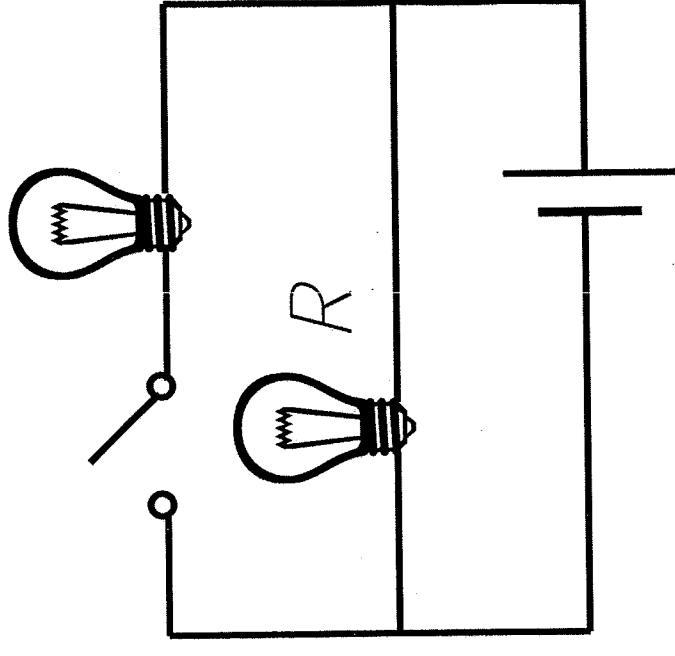- A) increases
- B) decreases
- C) remains unchanged

Interactive Question

A simple series circuit contains a resistance R and an ideal battery. If a second resistor is connected in parallel with R by closing the switch,



- A) the voltage across R will decrease.
- B) the voltage across R will increase.
- C) the total current in the circuit will increase.
- D) the equivalent resistance of the circuit will increase.

Problem: How much does it cost to run a 1200 W hair dryer for 10 minutes?

$$P = 1200 \text{ W}$$

$$\text{Energy} = 1.10 / \text{kW}\cdot\text{hr}$$

$$t = 10 \text{ min}$$

want money


$$\text{Money} = \frac{\text{Energy} \cdot \text{money}}{\text{Energy}}$$

$$= \text{Power} \cdot \text{time} \times \frac{\text{money}}{\text{Energy}}$$

$$(1200 \text{ W} \times 10 \text{ min}) \left(\frac{\$1.10}{\text{kW}\cdot\text{hr}} \right) \left(\frac{1 \text{ kW}}{1000 \text{ W}} \right) \left(\frac{60 \text{ min}}{1 \text{ hr}} \right) = .02$$

2 cents

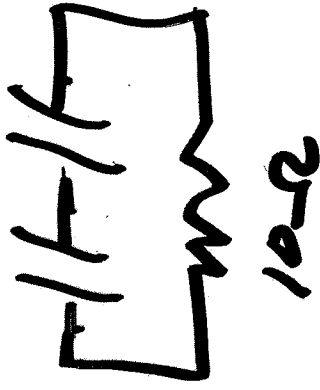Problem: A light bulb with a resistance of $10\ \Omega$ is placed in series with two 12 V batteries. How much power is dissipated by the bulb?



$$\mathcal{E} = 24\text{ V}$$

$$R = 10\ \Omega$$

want power

Power from batteries $P = I\mathcal{E}$

Power from bulb $P = I^2 R$

need to find I

$$\Delta V = \mathcal{E} = IR \quad I = \frac{\mathcal{E}}{R} = \frac{24\text{ V}}{10\ \Omega} = 2.4\text{ A}$$


$$A) \quad P = I\mathcal{E} = (2.4\text{ A})(24\text{ V}) = 57.6\text{ W}$$

$$B) \quad P = I^2 R = (2.4\text{ A})^2 (10\ \Omega) = 57.6\text{ W}$$

A

Interactive Question

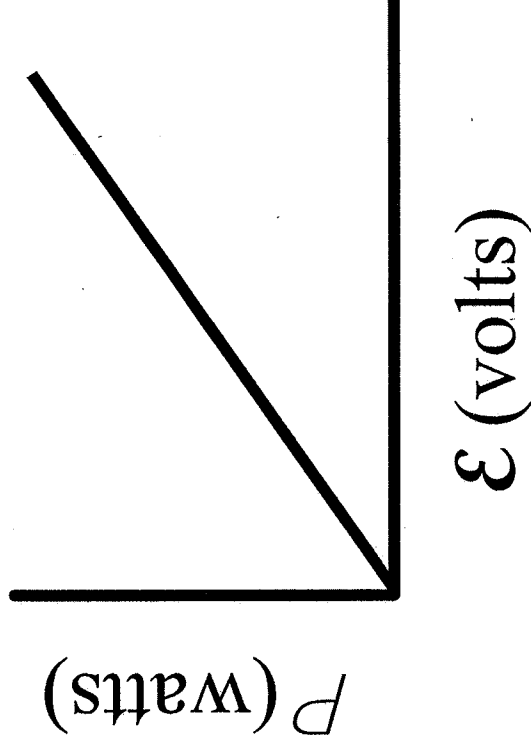In the graph shown, what physical quantity does the slope represent?



- A) Current
- B) Energy
- C) Voltage
- D) Resistance
- E) Power

Problem: A 4 amp current is maintained in a simple circuit with a total resistance of $2\ \Omega$. How much heat is generated in 3 seconds?

Given	$I = 4\text{ A}$	Want	Energy
	$R = 2\ \Omega$		
	$t = 3\text{ s}$		

$$\begin{aligned}\text{Energy} &= \text{power} \times \text{time} \\ &= (I^2 R) \times t \\ &= (4\text{ A})^2 (2\ \Omega) (3\text{ s}) = \underline{\underline{96\text{ J}}}\end{aligned}$$

Problem: A 100 W light bulb is designed to operate at 120 V ac.

- A) What is the effective current in the light bulb?
B) What is the resistance of the bulb?


Given 100 W

$\mathcal{E} = 120 \text{ V}$ want I

$$A) P = \mathcal{E}I \quad I = \frac{P}{\mathcal{E}} = \frac{100 \text{ W}}{120 \text{ V}} = \underline{.833 \text{ A}}$$

$$B) \Delta V = \mathcal{E} = IR \quad R = \frac{\mathcal{E}}{I} = \frac{120 \text{ V}}{.833 \text{ A}} = \underline{144 \Omega}$$

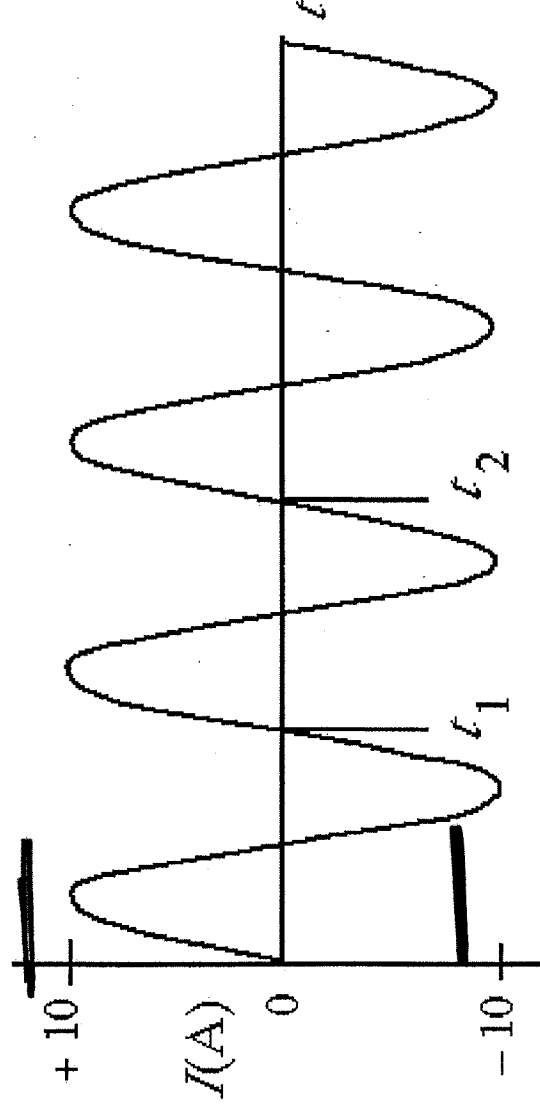Problem: The figure below shows the time variation of the current through the heating element of an iron when it is plugged into a standard ~~120 V~~, 60 Hz outlet. What is the (A) rms current and (B) resistance of the iron?



$$A) I_{RMS} = .707 I_{max} = (.707)(10A) = \underline{7.07A}$$

$$B) \mathcal{E} = IR \quad R = \frac{\mathcal{E}}{I} = \frac{120V}{7.07A} = \underline{17\Omega}$$