

Read 14.3

H.W Due today

Next H.W available

office hours 11:30-12:30


Review

$P = IE$ power battery

$P = I^2 R$ power resistor

Energy = power $\times$ time

AC power

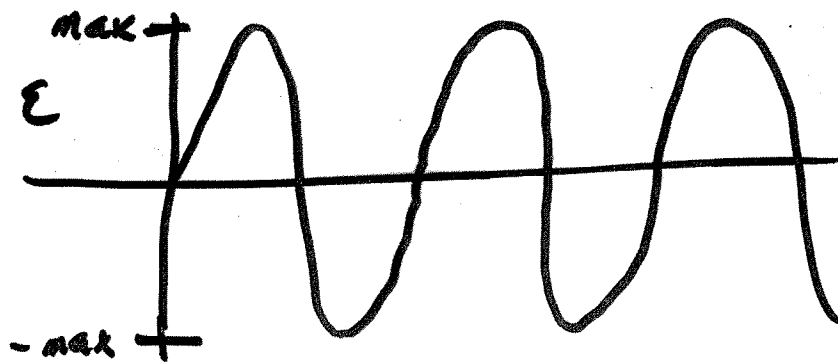


$$E_{RMS} = .707 E_{max}$$

$$I_{RMS} = .707 I_{max}$$

$$E_{RMS} = I_{RMS} R$$

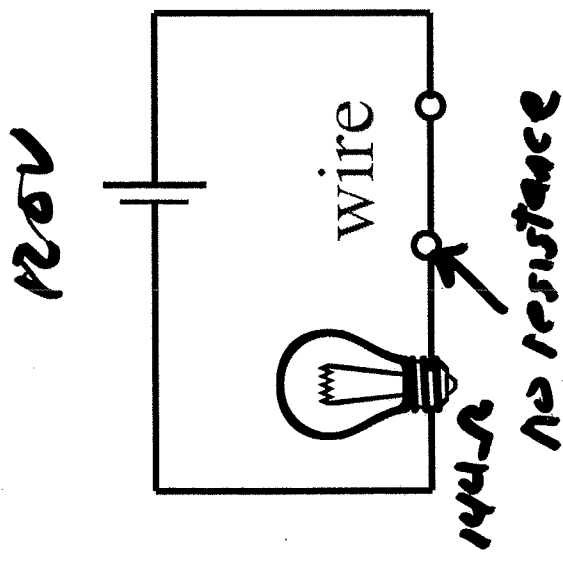
Problem: How many amps run through a tungsten wire when it is hooked up in series to a 100 watt light bulb and plugged into a 120 V electrical outlet? The light bulb has a resistance of $144\ \Omega$.



$$\mathcal{E} = I R$$

$$I = \frac{\mathcal{E}}{R} = \frac{120V}{144\ \Omega} = \underline{\underline{.83A}}$$

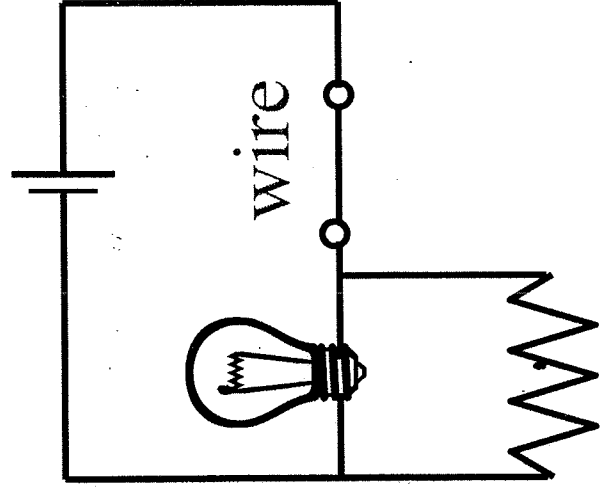Problem: How many amps run through a tungsten wire when it is hooked up in series to a 100 watt light bulb that is in parallel with a 600 W heater and plugged into a 120 V electric outlet?



The heater has a resistance of $24\ \Omega$ (which we can determine using $P = \mathcal{E}I$, and $\mathcal{E} = IR$ with $\mathcal{E} = 120\text{ V}$.) We already know the light bulb has a resistance of $144\ \Omega$.

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{144\ \Omega} + \frac{1}{24\ \Omega} = .486\ \Omega^{-1}$$

$$\underline{R_{\text{eq}}} = 20.5\ \Omega = \frac{1}{.486}$$

$$I = \frac{\mathcal{E}}{R_{\text{eq}}} = \frac{120\text{ V}}{20.5\ \Omega} = 5.8\text{ A}$$



Problem: What if 600 W heater is replaced with a 740 W heater with a resistance of 19.5Ω ?

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{44 \Omega} + \frac{1}{19.5 \Omega} = .0582 \Omega^{-1}$$

$$\frac{1}{R_{eq}} = .0582 \Omega^{-1} \quad R_{eq} = \underline{17 \Omega}$$
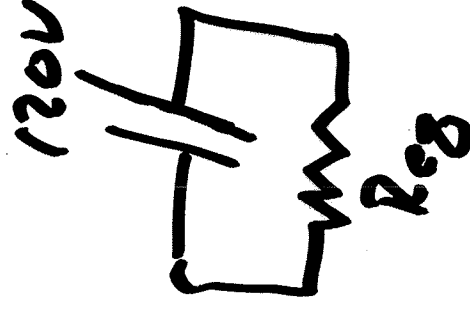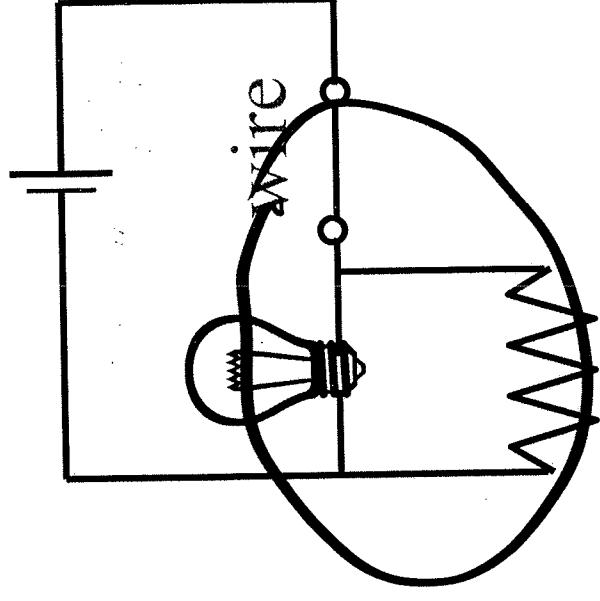
$$I = \frac{\mathcal{E}}{R_{eq}} = \frac{120V}{17 \Omega} = \underline{7.0 A}$$



Interactive Question

At 120 V, which has a larger resistance, a 100 W light bulb or a 60 W light bulb?

- A) 100 W
- B) 60 W
- C) They both have the same resistance

A



Interactive Question

If a 100 W light bulb is placed in series with a 60 W light bulb (instead of in parallel as they were designed for), which will burn brighter?

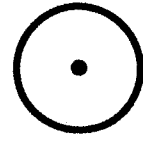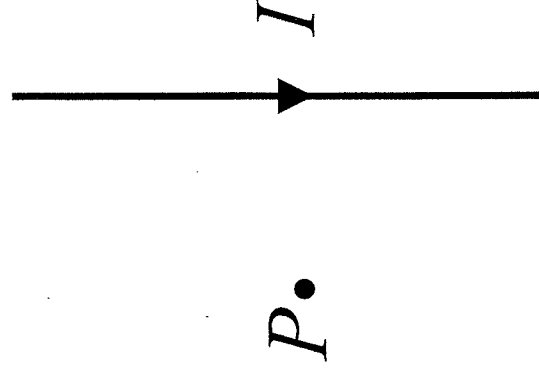- A) 60 W
- B) 100 W
- C) The same
- D) It depends on the order of the bulbs

Interactive Question

A long straight wire has a current going in the direction shown in the figure to the right. Which direction is the magnetic field at point P ?




(A)



(B)



(C)

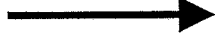


(D)

E) None of the above

Interactive Question

A long straight wire has a current going in the direction shown in the figure to the right. Which direction is the magnetic field at point P ?

$P \bullet \otimes I$

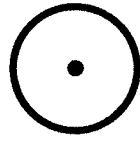

(A)



(B)



(C)



(D)

E) None of the above

(C)